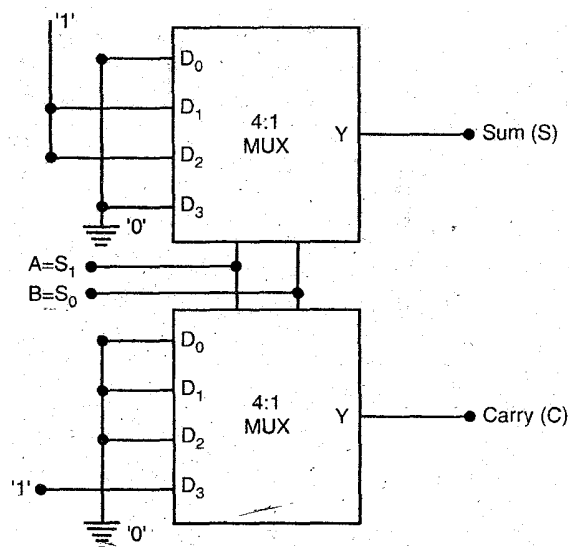


## EXAMPLE

1. implement half adder circuit using 4 : 1 MUX or multiplexers only.

Ans. Truth table of half adder is as shown:

Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



2. Implement using 4: 1 MUX


$$F = \sum m(0, 3, 4, 7)$$

Ans. The implementation table is as shown:

	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
$\bar{A}$	0	1	2	3
A	4	5	6	7

[ 1    0    0    1 ] Inputs to Multiplexer

Implementation:

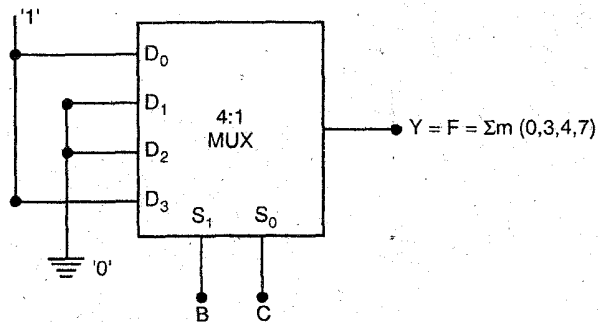


3. How many select lines are there for a 30 to 1 MUX?

Ans. For 30: 1 MUX, 5 select lines are required. 4 select lines are for 16 : 1 MUX's and

1 select line for 2: 1 MUX.  $2^n = M$  formula is used. Where n = number of select lines and M are the number of inputs for a MUX.

= 32. Thus, 5 select lines are needed.

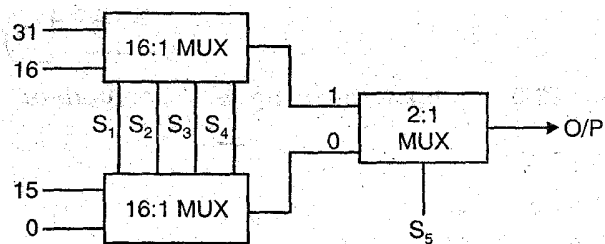

4. Implement using 4 x 1 MUX

$$F = \sum m(0, 3, 4, 7)$$

Ans.

